

Chapter 4: Logic gates and logic circuits

Terms:

- Logic proposition/assertion: Statement that can be either TRUE or FALSE.
- Boolean variables can be either TRUE or FALSE.
- Logic gates are circuits that work with Boolean values.
- Logic circuits are combination of logic gates.
- Truth tables show relation between input and output of logic circuits.

Boolean Operators and symbols and logic gates:

YES



INPUT		OUTPUT
A		
0		0
1		1

NOT



INPUT		OUTPUT
A		
0		1
1		0

AND



INPUT		OUTPUT
A	B	
0	0	0
1	0	0
0	1	0
1	1	1

OR



INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	1

XOR



INPUT		OUTPUT
A	B	
0	0	0
1	0	1
0	1	1
1	1	0

NAND



INPUT		OUTPUT
A	B	
0	0	1
1	0	1
0	1	1
1	1	0

NOR



INPUT		OUTPUT
A	B	
0	0	1
1	0	0
0	1	0
1	1	0

XNOR



INPUT		OUTPUT
A	B	
0	0	1
1	0	0
0	1	0
1	1	1